



AMERICAN INTERNATIONAL UNIVERSITY- BANGLADESH (AIUB)

Introduction to Electrical Circuit

FALL 2023-2024

Section: L, Group: 07

LAB REPORT ON

Study of 'Nodal Analysis' in R-L-C combination circuit in AC

Supervised By

MD. SHAHARIAR PARVEZ

Name	ID
1.MD. Abdullah	22-48065-2
2.Azmir Islam Kafi	22-47981-2
3.Mohammad Ansar Uddin	22-47975-2
4.Chinmoy Guha	22-48056-2
5.Suvra Chakraborty	22-48067-2

Abstract:

The purpose of the experiment was to develop an understanding of the method of determining voltage and current using 'Nodal Analysis' in an R-L-C AC circuit. Circuits containing R, L, and C components were constructed, and the objective was to analyze the outputs of R-L-C series-parallel combination circuits to obtain practical values as well as simulated or theoretical results. Additionally, the experiment involved determining the phase relationship between V and I in an R-L-C combination circuit and drawing a complete vector diagram to comprehend the method of using Nodal analysis.

Circuit diagram:

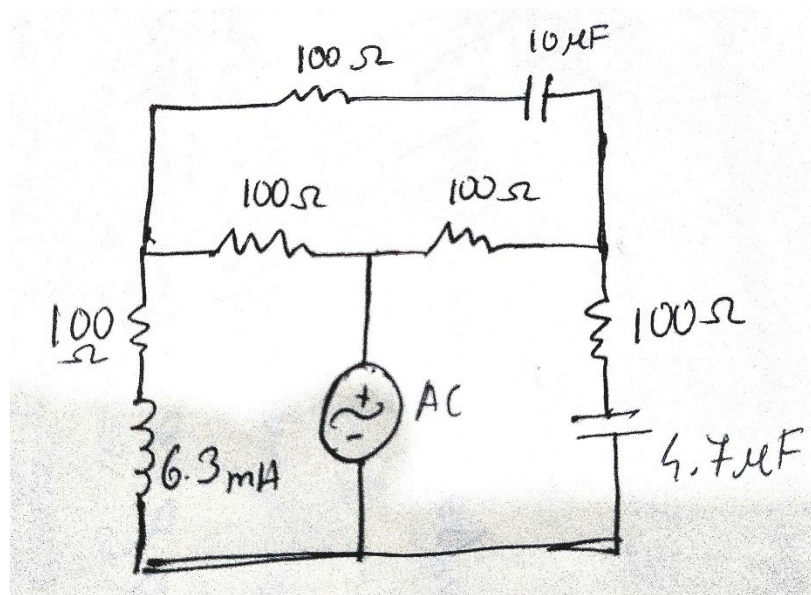


Figure 1: Circuit diagram for Nodal Analysis

Apparatus:

- a) Oscilloscope, b) Function generator c) Resistor: 100 ohm - 5 pcs d) Inductor: 6.3 mH e) Capacitor: 4.7 microF and 10 microF, f) Connecting wire, g) Bread board

Experimental Procedure:

The circuit illustrated in Fig. 1 was successfully constructed, with channel 1 of the oscilloscope connected across the function generator and channel 2 across R2. The amplitude of the input signal was set at 10V peak, and the frequency was adjusted to 1 kHz, with a sinusoidal wave shape selected. Measurements were taken for the values of V_A and the current I_{V A-B}. The phase relationship between the supply voltage V and the node voltage at V_A was determined. Subsequently, channel 2 of the oscilloscope was connected across R3, and the phase relationship between the waves was determined. The values of V_C and I_{V B-C} were measured, and the phase relationship between the supply voltage V and the node voltage at V_C was determined. Further analysis involved determining I_{V A-C}, I_{V A-G}, and I_{V C-G}. All the obtained currents were compared with their theoretical values, and the percentage error was calculated for comprehensive assessment..

Result analysis :

Data Table:

Freq.(f) (kHz)	Supply Voltage (V)	Practical Value										Error
		I _{V B-A}		I _{V B-C}		I _{V A-C}		I _{V A-G}		I _{V C-G}		%Error= (Theoretical – Practical value/Theoretical value) *100
		Mag. I _{V B-A} (mA)	Phase θ (°)	Mag. I _{V B-C} (mA)	Phase θ (°)	Mag. I _{V A-C} (mA)	Phase θ (°)	Mag. I _{V A-G} (mA)	Phase θ (°)	Mag. I _{V C-G} (mA)	Phase θ (°)	%
1kHz	7.07V rms	66.9 64	- 3.3 4	68. 21 2	- 3.3 4	134 .60 5	1.2	69. 874	- 24.7 4	69.7 31	15.2	5%

Simulation:


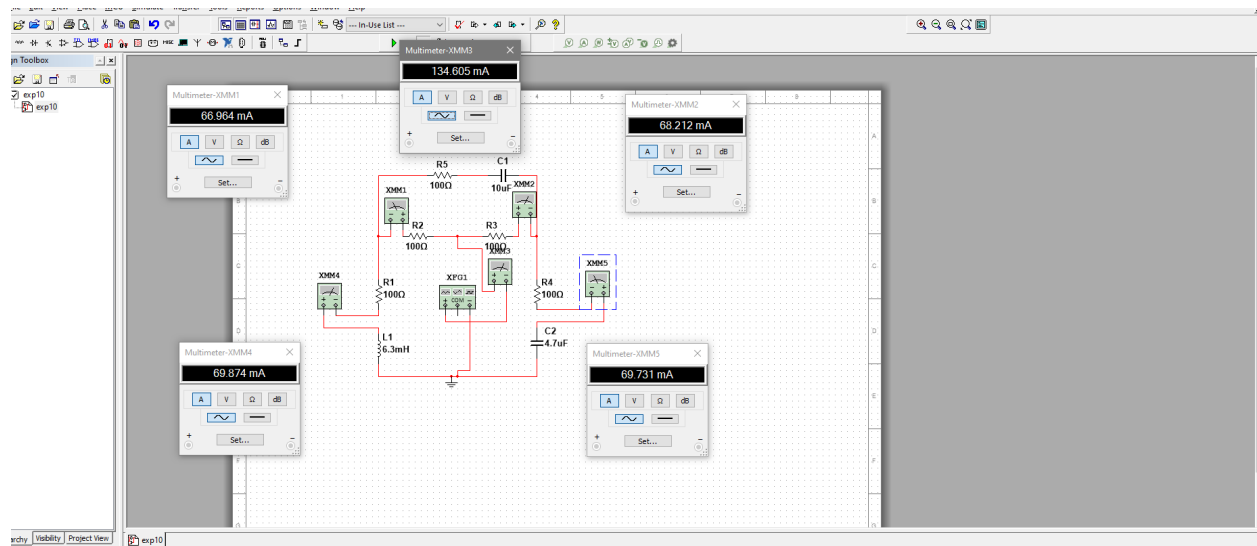


Figure: Currents for the circuit.

Calculation:



$$R_2 \parallel R_3 = 50 \Omega$$
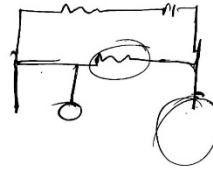
$$X_L = \frac{1}{2\pi \times 1000 \times 10 \times 10^{-6}} = 15.9 \Omega$$



$$Z_{RC} = 100 - 15.9j \Omega$$
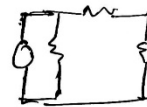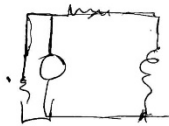
$$R_{23} \parallel Z_{RC} = \frac{(50)(100 - 15.9j)}{50 + 100 - 15.9j} = 33.52 - 1.75j$$



$$R_{23} \parallel Z_{RC}$$

$$X_L = \frac{1}{2\pi \times 1000 \times 6.7 \times 10^{-6}} = 33.86 \Omega$$

$$Z_{RC2} = 100 - 33.86j \Omega$$

$$R_{23} \parallel Z_{RC} + Z_{RC2} = (33.52 - 1.75j + 100 - 33.86j) \Omega = 133.52 - 35.61j$$

$$(R_{23} \parallel Z_{RC} + Z_{RC2}) \parallel Z_{RC} \quad X_L = 2\pi fL = 2\pi \times 1000 \times 6.3 \times 10^{-3} = 39.58 \Omega$$

$$Z_{R5} = 100 + 39.58 \Omega$$

$$(R_{23} \parallel Z_{R_C} + Z_{R_L}) \parallel Z_{R_L} = \frac{(133.52 - 35.61j)(100 + 39.58j)}{133.52 - 35.61j + 100 + 39.58j}$$

$$Z_T = 63.32 + 6.3j \Omega$$

$$I_s = \frac{7.07}{63.22 + 6.3j \Omega} = 0.11 - 0.011j$$

$$I_{R_2} = \frac{Z_T}{R_L} \times I_s = \frac{63.22 + 6.3j \Omega}{100} \times 0.11 - 0.011j$$

$$= 0.07 \angle -3.34^\circ$$

$$I_{R_3} = \frac{Z_T}{R_3} \times I_s = 0.069 \angle -3.34^\circ$$

$$I_{R_{23}} = \frac{Z_T}{R_{23}} \times I_s = 0.14 \angle 1.2^\circ$$

$$I_{Z_L} = \frac{Z_T}{Z_L} \times I_s = 0.069 \angle -24.74^\circ$$

$$I_{R_{L_2}} = \frac{Z_T}{Z_{R_{L_2}}} \times I_s = 0.063 \angle 15.2^\circ$$

Discussion

The purpose of the experiment was to develop an understanding of the method of determining voltage and current using 'Nodal Analysis' in an R-L-C AC circuit. Circuits containing R, L, and C components were constructed, and the objective was to analyze the outputs of R-L-C series-parallel combination circuits to obtain practical values as well as simulated or theoretical results. Additionally, the experiment involved determining the phase relationship between V and I in an R-L-C combination circuit. All of these were successfully demonstrated and found. The phase of each I was calculated through theoretical calculations and we found that there was a bit of a difference between the calculated values and practical values.

Conclusion:

By completing this experiment we had become familiar with the method of determining voltage and current using Nodal Analysis in an RLC AC circuit.