



AMERICAN INTERNATIONAL UNIVERSITY- BANGLADESH (AIUB)

Introduction to Electrical Circuit

FALL 2023-2024

Section: L, Group: 07

LAB REPORT ON

Transient Analysis of RC Series and RL series using MULTISIM

Supervised By

MD. SHAHARIAR PARVEZ

Name	ID
1.MD. Abdullah	22-48065-2
2.Azmir Islam Kafi	22-47981-2
3.Mohammad Ansar Uddin	22-47975-2
4.Chinmoy Guha	22-48056-2
5.Suvra Chakraborty	22-48067-2

Abstract:

Multism serves as a comprehensive electrical circuit simulation tool that enables the creation, validation, and simulation of circuits to determine unknown parameter values and generate graphs. The software includes a library of components and devices that can be employed for constructing, simulating, and illustrating various circuit configurations.

The objective of this exercise was to learn about-

1. Simulation of circuits by using components from the Multisim library
2. Simulation of circuits by writing script files and to analyze obtained graphs and results.

Circuit diagram:

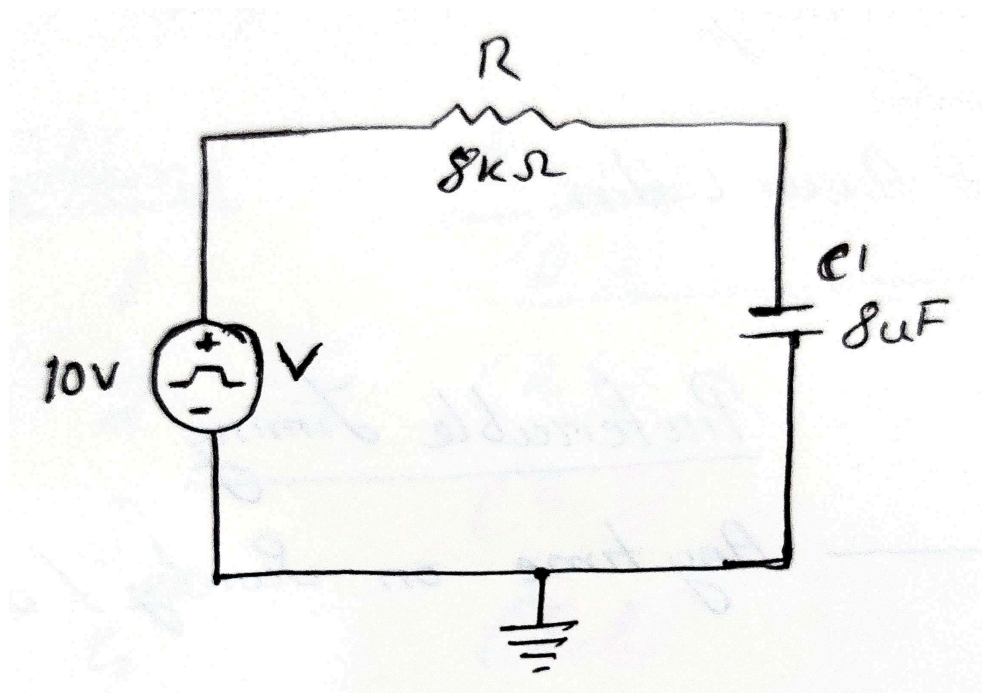


Figure 1: RC circuit

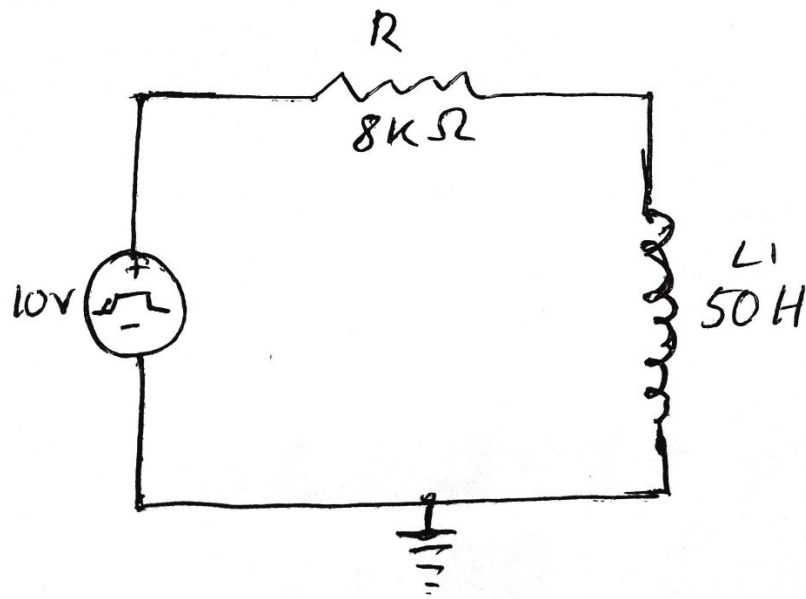


Figure 2: RL circuit

Apparatus:

1. PC.
2. Multisim Software.

Experimental Procedure:

The process began by opening the Multisim software window through the sequence Start → Program → Multisim. Subsequently, the component window was accessed from the menu bar using the path Place → Components. Various components such as a DC source, digital clock, step voltage source, resistor, capacitor (for RC), or an inductor (for RL) were selected from the components menu, along with a ground source. Clock or pulse voltage sources were incorporated through Place → Components → Sources → Signal_Voltage_Sources → Clock_Voltage or Pulse_Voltage. The parameters for the sources, resistors, and capacitors/inductors were appropriately configured. The circuit elements were interconnected using wires and labeled accordingly. Moving to the Analysis and Simulation bar, the setting was changed to Transient through Analysis and Simulation → Transient, with initial conditions set to zero. A suitable end time, ensuring visibility of multiple wave cycles but preventing excessive cycles, was selected. Output variables were chosen through Analysis and Simulation → Output → Add output variable, and additional expressions were inserted if necessary via Analysis and Simulation → Output → Add expression. The simulation was then executed for the designed circuit, and the output was analyzed using the simulation grapher view as instructed.

Result analysis :

Table 1:

For RC series circuit,

Time (t)	Value Time Constant	% Charged	V _c
τ	64ms	63%	6.3
2τ	128ms	86%	8.6
3τ	192ms	95%	9.5
4τ	256ms	98%	9.8
5τ	320ms	99%	9.9

Table 2:

For RL series circuit,

Time (t)	Value Time Constant	% Storage	I _L
τ	6.25ms	63.2%	0.79uA
2τ	12.5ms	86%	1.08uA
3τ	18.75ms	95%	1.187uA
4τ	25ms	98%	1.227uA
5τ	31.25ms	99%	1.24uA

Simulation:

TABLE 1:

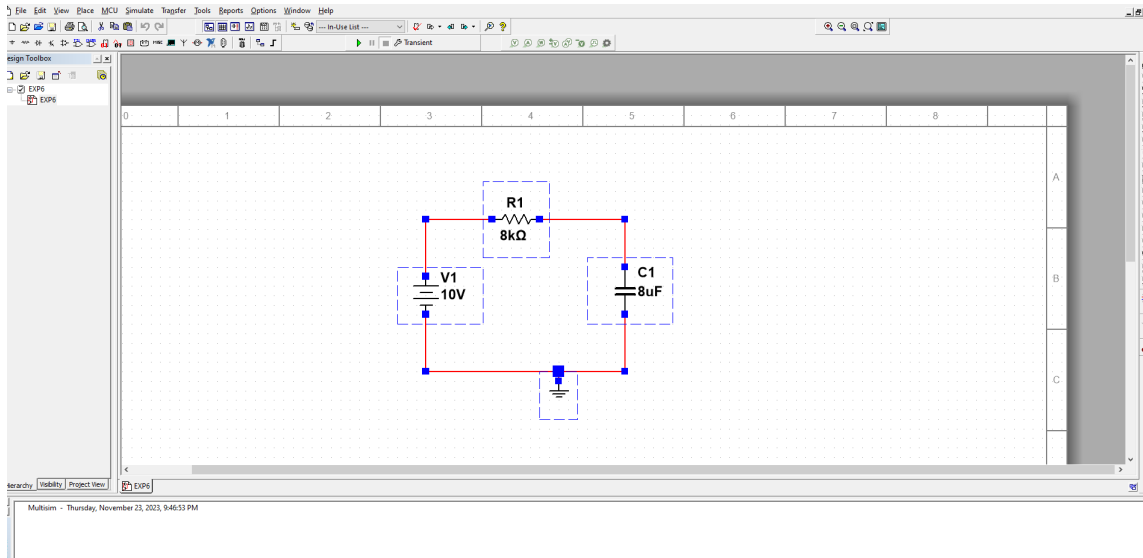


Figure: RC Circuit.

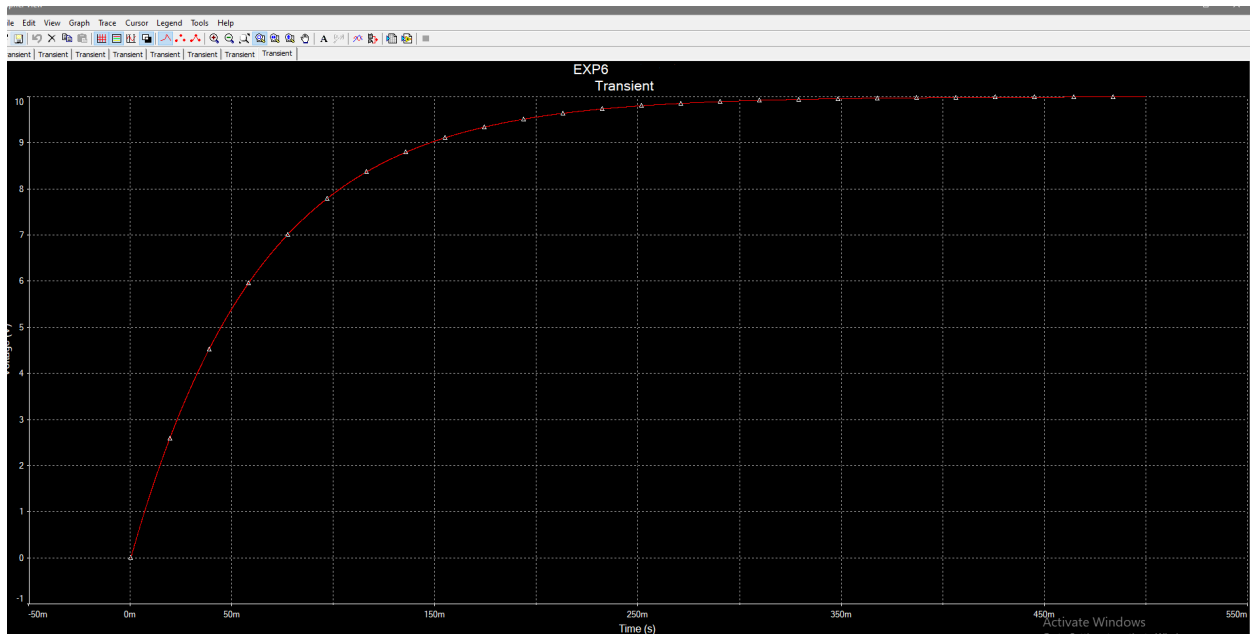


Figure: RC graph.

TABLE 2:

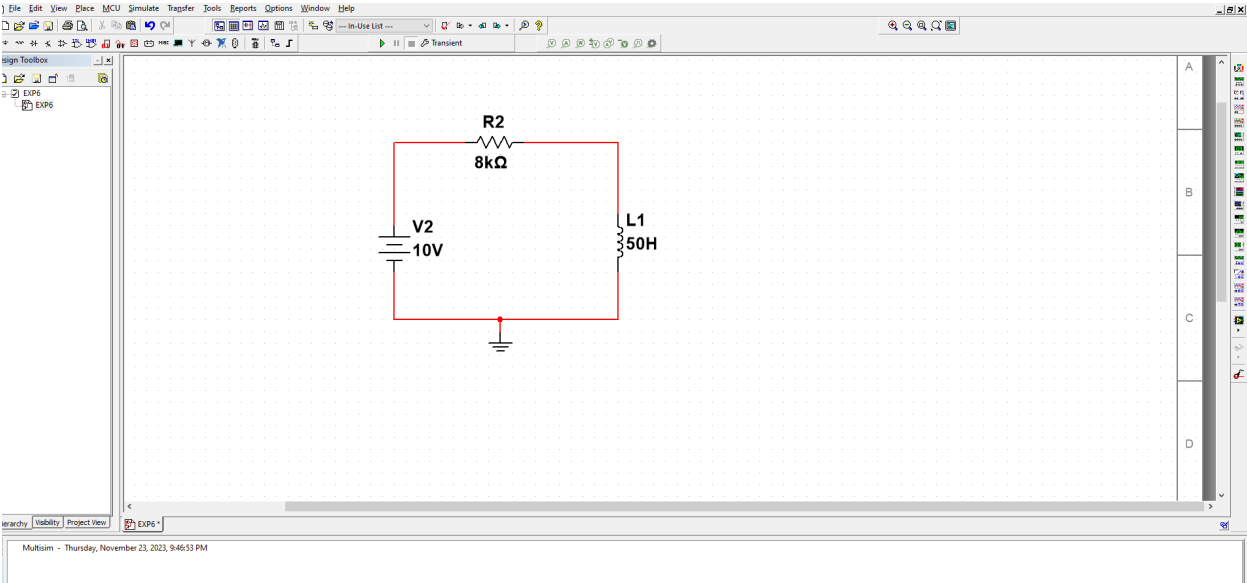


Figure: RL Circuit.

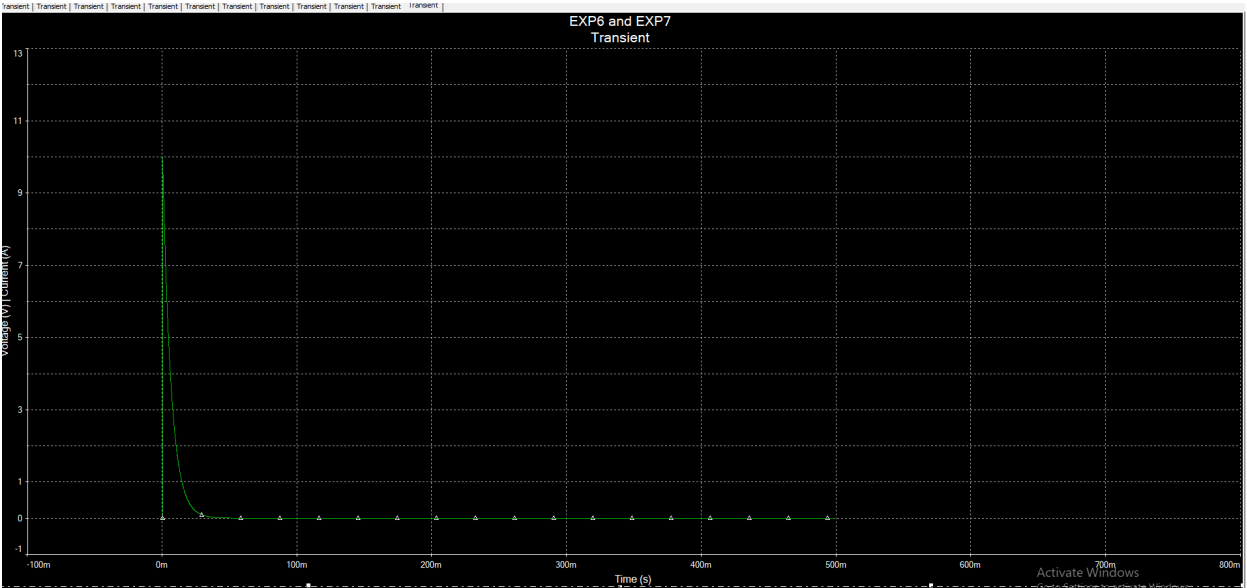


Figure: RL Graph

Calculation:

For Table 1:

Time Constant = $RC = 64\text{ms}$

$1T = 64\text{ms}$

$2T = 128\text{ms}$

$3T = 192\text{ms}$

$4T = 256\text{ms}$

$5T = 320\text{ms}$

V_c readings were taken from the simulation.

% charged:

$1T = 6.3/10 * 100\%$

$2T = 86\%$

$3T = 95\%$

$4T = 98\%$

$5T = 99\%$

For Table2:

Time Constant = $L/R = 6.25\text{ms}$

$1T = 6.25\text{ms}$

$2T = 12.5\text{ms}$

$3T = 18.75\text{ms}$

$4T = 25\text{ms}$

$5T = 31.25\text{ms}$

i_L readings were taken from the simulation.

% charged:

$1T = 0.79/1.25 * 100\% = 63\%$

$2T = 86\%$

$3T = 95\%$

$4T = 98\%$

$5T = 99\%$

Discussion

The complete experiment was done with Multisim software and the simulation values do match with the calculations that can be done with the formulae.

Conclusion:

Transient Analysis of RC Series and RL series using MULTISIM completed successfully.